

# Number Representation and Computer Arithmetic

University of South Carolina

Introduction to Computer Architecture

Fall, 2024

Mehdi Yaghouti



**Molinaroli College of  
Engineering and Computing**

UNIVERSITY OF SOUTH CAROLINA

# Binary Number Representation

- **Decimal system:**

- Base: 10
- Digits:  $\{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$
- Representation of a decimal number:

1's column  
10's column  
100's column  
1000's column

$$9742_{10} = 9 \times 10^3 + 7 \times 10^2 + 4 \times 10^1 + 2 \times 10^0$$

nine          seven          four          two  
thousands    hundreds    tens          ones

- **Binary system:**

- Base: 2
- Digits:  $\{0, 1\}$
- Representation of a binary number:

1's column  
2's column  
4's column  
8's column  
16's column

$$10110_2 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 22_{10}$$

one          no          one          one          no  
sixteen    eight      four      two      one

# Unsigned Binary Numbers

- N-bit binary number can represent  $2^N$  numbers,

- Minimum:  $\overbrace{0 \dots 0}^{\text{N-bits}}$
- Maximum:  $\overbrace{1 \dots 1}^{\text{N-bits}}$
- Range:  $[0, \dots, 2^N - 1]$

- Decimal to binary conversion

- Using common powers of 2  
1, 2, 4, 8, 16, 32, 64, 128, 256, 512, 1024, 2048, 4096
- Repeated Divisions

- Binary to decimal conversion

$$(b_N \dots b_0)_2 = \sum_{k=0}^N 2^k b_k$$

4-Bit Binary Numbers	Decimal Equivalents
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

# Hexadecimal Representation

- **Hexadecimal system:**

- Base: 16
- Digits:  $\{0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F\}$
- Representation of a hexadecimal number:

1's column  
16's column  
256's column

$$2ED_{16} = 2 \times 16^2 + E \times 16^1 + D \times 16^0 = 749_{10}$$

two                  fourteen                  thirteen  
two hundred fifty six's      sixteen                  ones

- Correspondence between Hex digits and 4-bits

$$\sum_{k=0}^N 2^k b_k = \sum_{k=0}^{N/4} 16^k \left( \sum_{l=0}^3 2^l b_{(4*k+l)} \right)$$

- Binary to Hexadecimal conversion

- Pack each 4-bit into a hex digit

- Hexadecimal to Binary conversion

- Unpack each hex digits into 4-bits

**DEAFDAD8 = 1101 1110 1010 1111 1101 1010 1101 1000**

Hexadecimal Digit	Binary Equivalent
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
A	1010
B	1011
C	1100
D	1101
E	1110
F	1111

# Octal Representation

- **Octal system:**

- Base: 8
- Digits: {0, 1, 2, 3, 4, 5, 6, 7}
- Representation of an octal number:

1's column  
8's column  
64's column

$$367_8 = \underbrace{3}_{\substack{\text{three} \\ \text{sixty fours}}} \times 8^2 + \underbrace{6}_{\substack{\text{six} \\ \text{eights}}} \times 8^1 + \underbrace{7}_{\substack{\text{seven} \\ \text{ones}}} \times 8^0 = 247_{10}$$

Octal Digit	Binary Equivalent
0	000
1	001
2	010
3	011
4	100
5	101
6	110
7	111

- Correspondence between Octal digits and 3-bits

$$\sum_{k=0}^N 2^k b_k = \sum_{k=0}^{N/3} 8^k \left( \sum_{l=0}^3 2^l b_{(3*k+l)} \right)$$

- Binary to Octal conversion

- Pack each 3-bit into a octal digit

- Octal to Binary conversion

- Unpack each octal digits into 3-bits

$$(2357)_8 = 010 \ 011 \ 101 \ 111$$

# Binary Addition

- **Basic Rules:**

- $0 + 0 = 0$
- $0 + 1 = 1$
- $1 + 0 = 1$
- $1 + 1 = 10$  (0 with a carry of 1)

- **Steps for Adding Two Binary Numbers:**

- 1 Aligning the Numbers
- 2 Adding digit by digit, starting from LSB
- 3 Carry Over: If the sum is 2 (binary 10), carry the 1 to the next column
- 4 Overflow: The carry out of the leftmost digit

$$\begin{array}{r} \phantom{+} 11\ 1 \\ \phantom{+} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$

- Care must be taken as registers have constant number of bits

# Binary Subtraction

- **Basic Rules:**

- $0 - 0 = 0$
- $1 - 0 = 1$
- $1 - 1 = 0$
- $0 - 1 = 1$  (with a borrow of 1 from the next higher bit)

- **Steps for Subtracting Two Binary Numbers:**

- 1 Aligned the numbers
- 2 Subtracting digit by digit, starting from LSB
- 3 Borrowing: When subtracting 1 from 0, borrow 1 from the next higher bit
- 4 Borrow in: If a borrow needed beyond the leftmost digit, the result is negative

$$\begin{array}{r} \overset{1}{\phantom{0}} \\ 0101 \\ - 1101 \\ \hline 0000 \end{array}$$

# Sign/Magnitude Number System

- **Sign/Magnitude:**

- Sign bit: Most significant bit

$$\begin{cases} + \rightarrow 0 \\ - \rightarrow 1 \end{cases}$$

Example:

$$+23 = 00010111$$

$$-23 = 10010111 \quad (\text{sign/magnitude representation})$$

- Spans the range  $[-(2^{N-1} - 1), 2^{N-1} - 1]$
- Ordinary addition doesn't work on sign included representation
- Zero has two representations  $+0, -0$
- Troublesome to use in fast arithmetic circuits



# Two's Complement Number System

-8	4	2	1

- **Two's Complement system:**

- $N$ -bits Two's complement representation

$$(b_{N-1} \dots b_0)_2 = -b_N 2^{N-1} + \sum_{k=0}^{N-2} 2^k b_k$$

- Spans the asymmetric range  $[-2^{N-1}, 2^{N-1} - 1]$
- **Ordinary addition works well on sign included representation**
- Sign bit: Most significant bit

$$\begin{cases} + \rightarrow 0 \\ - \rightarrow 1 \end{cases}$$

- Zero has only one representation
- Two's complement is the most accepted one for fast arithmetic circuits

Decimal Representation	Twos Complement Representation
+8	—
+7	0111
+6	0110
+5	0101
+4	0100
+3	0011
+2	0010
+1	0001
0	0000
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

# Two's Complement System

## ● Negation Rule

- 1 Negate all the bits
- 2 Add 1

Example:

$$+23 = 00010111 \xrightarrow{\text{negated}} 11101000 \xrightarrow{+1} 11101001 = -23$$

$$-23 = 11101001 \xrightarrow{\text{negated}} 00010110 \xrightarrow{+1} 00010111 = +23$$

## ● Addition/Subtraction

$$47 + 11 = 58$$

$$\begin{array}{r} 00101111 \\ + 00001011 \\ \hline 00111010 \end{array}$$

$$47 - 11 = 36$$

$$\begin{array}{r} 00101111 \\ + 11110101 \\ \hline 100100100 \end{array}$$

$$-47 + 11 = -36$$

$$\begin{array}{r} 11010001 \\ + 00001011 \\ \hline 11011100 \end{array}$$

$$-47 - 11 = -58$$

$$\begin{array}{r} 11010001 \\ + 11110101 \\ \hline 111000110 \end{array}$$

# Overflow

- **Unsigned Numbers**

- Overflow occurs when there is a carry out of the MSB column

Example:

$$7 + 12 = 19$$

$$\begin{array}{r} 0111 \\ + 1100 \\ \hline 11011 \end{array}$$

- **Signed Numbers (Two's complement)**

- Overflow can only happen when two numbers have the same sign bit
- Overflow occurs when the result has the opposite sign bit

Example:

$$7 + 4 = 11$$

$$\begin{array}{r} 0111 \\ +0100 \\ \hline 1011 \end{array}$$

$$-7 - 4 = -11$$

$$\begin{array}{r} 1001 \\ + 1100 \\ \hline 10101 \end{array}$$

# Adder



- **Half Adder:**  $\{c_{out}, S\} = A + B$

A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

## Half Adder

  


# Adder

- **Half Adder:**  $\{c_{out}, S\} = A + B$
- **Full Adder:**  $\{c_{out}, S\} = A + B + c_{in}$
- **Generate:**  $G = A \bullet B$
- **Propagate:**  $P = A \oplus B$

**Full Adder**

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
 
$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$




# Adder

- **Half Adder:**  $\{c_{out}, S\} = A + B$
- **Full Adder:**  $\{c_{out}, S\} = A + B + c_{in}$
- **Generate:**  $G = A \bullet B$
- **Propagate:**  $P = A \oplus B$
- **Delay:**  

$$\max\{2t_{pd\_xor}, t_{pd\_xor} + t_{pd\_or} + t_{pd\_and}\}$$


**Full  
Adder**

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

 

# Adder

- **Half Adder:**  $\{c_{out}, S\} = A + B$
- **Full Adder:**  $\{c_{out}, S\} = A + B + c_{in}$
- **Generate:**  $G = A \bullet B$
- **Propagate:**  $P = A \oplus B$
- **Delay:**  




$$\max\{2t_{pd\_xor}, t_{pd\_xor} + t_{pd\_or} + t_{pd\_and}\}$$
- $t_{FA} = t_{pd\_or3} + t_{pd\_and}$

**Full Adder**

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

   

# SystemVerilog (Optional)

- Implementation using P and G signals


```
module fulladder( input  logic a, b, cin,
                 output logic s, cout );

    logic p, g;

    assign  p = a ^ b;
    assign  g = a & b;

    assign  s = p ^ cin;
    assign cout = g | (p & cin);

endmodule
```

 


- The second alternative

```
module fulladder( input logic a, b, cin,
                 output logic s, cout );

    assign  s = cin ^ (a ^ b);
    assign cout = a & b | cin & a | cin & b;

endmodule
```

 




# Ripple-Carry Adder

- **Carry Propagate Adder (CPA):** Sums N-bit inputs
- **Ripple-Carry Adder:** Chains N full adders
- **Delay:**  $t_{pd\_rca} = N_t t_{FA}$




Full Adder

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

   

# Look-ahead Block

- **Generate:**

$$G_{j:i} = G_j + P_j G_{j-1:i}$$

- **Propagate:**

$$P_{j:i} = P_j P_{j-1} \dots P_i$$




- **Carry:**

$$C_{out} = G_{j:i} + P_{j:i} C_{in}$$

- **Delay:**


$$t_{pg} = \max\{t_{AND}, t_{XOR}\}$$

$$t_{pg\_block} = 3 (t_{AND} + t_{OR})$$

   


 
# Carry Look-Ahead Adder

- **Generate:**  $G_{j:i} = G_j + P_j G_{j-1:i}$
- **Propagate:**  $P_{j:i} = P_j P_{j-1} \dots P_i$
- **Delay:**  $t_{cla} = t_{pg} + t_{pg\_block} + \left(\frac{N}{k} - 1\right) t_{and\_or} + k t_{FA}$




 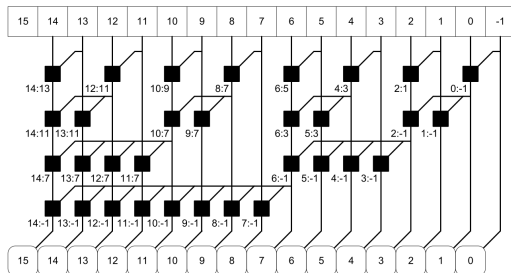
# Prefix Adder (Optional)

- **Generate:**  $G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$
- **Propagate:**  $P_{i:j} = P_{i:k} P_{k-1:j}$
- **Delay:**  $t_{PA} = t_{pg} + t_{pg\_prefix} \log_2 N + t_{XOR}$



$i,j$

  

# Question


- Compare the delays of a 64-bit ripple-carry, a 64-bit carry-lookahead with 4-bit blocks and a 64-bit prefix adder.

Gate	$t_{pd}$ (ps)	$t_{cd}$ (ps)
NOT	15	10
2-input NAND	20	15
3-input NAND	30	25
2-input NOR	30	25
3-input NOR	45	35
2-input AND	30	25
3-input AND	40	30
2-input OR	40	30
3-input OR	55	45
2-input XOR	60	40
 
# SystemVerilog (Optional)


- keyword parameter
- Using high level description we leave the implementation to the synthesizer

```
module adder #(parameter N = 8) ( input logic [N-1:0] a, b,  
                                  input logic cin,  
                                  output logic [N-1:0] s,  
                                  output logic cout);  
  
    assign {cout, s} = a + b + cin;  
  
endmodule
```




 
# Subtraction

- **Two's Complement**
- **Subtraction:**  $A - B = A + \overline{B} + 1$


  
# Comparators

- Compares two binary inputs
- Using XNOR to check equality
- Using subtraction and check the sign bit





# Multiplication

- Binary multiplication is based on two basic operations:
  - Generation of partial products
  - Accumulation
- The multiplication of two  $N$ -bits number is in general a  $2N$ -bits number

$$\begin{array}{r} \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \times \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \\ \hline \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \\ + \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \phantom{0} \\ \hline \textcolor{blue}{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{1} \phantom{0} \phantom{0} \end{array}$$

# Multiplication


- Binary multiplication is based on two basic operations:
  - Generation of partial products
  - Accumulation
- The multiplication of two N-bits number is a 2N-bits number in general
- Each partial product is either zero or the multiplicand

$$\begin{array}{rcccccccc} & & & A_3 & A_2 & A_1 & A_0 & & \\ & & & B_3 & B_2 & B_1 & B_0 & & \\ x & & & & & & & & \\ \hline & & & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 & & \\ & & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 & & & \\ & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 & & & & \\ + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 & & & & \\ \hline P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0 & \end{array}$$
 
# Array Multiplier

- Binary multiplication is based on two basic operations:
  - Generation of partial products
  - Accumulation
- The multiplication of two N-bits number is a 2N-bits number in general
- Each partial product is either zero or the multiplicand
- Partial products can be generated by using AND gates

$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$



## Sequential Multiplier (Optional)

- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero of the multiplicand
  - The partial products can be accumulated incrementally
- It can be best understood by an example

$$\begin{array}{r} M: \qquad \qquad \qquad 1 \ 1 \ 0 \ 1 \\ Q: \qquad \qquad \qquad \qquad \qquad \qquad 1 \ 1 \ 1 \ 0 \\ \hline ACC: \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

# Sequential Multiplier (Optional)

- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero of the multiplicand
  - The partial products can be accumulated incrementally
- It can be best understood by an example

$$\begin{array}{r} M: \quad 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\ Q: \quad \quad \quad \quad \quad \quad \quad \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad \quad \quad 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\ ACC: \quad 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\ \hline ACC': \quad 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

# Sequential Multiplier (Optional)

- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero of the multiplicand
  - The partial products can be accumulated incrementally
- It can be best understood by an example

$$\begin{array}{r} M: \quad 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\ Q: \quad \quad \quad \quad \quad \quad \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad \quad \quad 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\ ACC: \quad 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\ \hline ACC': \quad 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \end{array}$$

# Sequential Multiplier (Optional)

- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero of the multiplicand
  - The partial products can be accumulated incrementally
- It can be best understood by an example

$$\begin{array}{r} M: \quad 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\ Q: \quad \quad \quad \quad \quad \quad \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad \quad 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \\ ACC: \quad 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\ \hline ACC': \quad 0 \ 1 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \end{array}$$

# Sequential Multiplier (Optional)


- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero of the multiplicand
  - The partial products can be accumulated incrementally
- It can be best understood by an example

$$\begin{array}{r} M: \quad 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \\ Q: \quad \quad \quad \quad \quad \quad \quad \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad \quad 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \\ ACC: \quad 0 \ 1 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \\ \hline ACC': \quad 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \end{array}$$



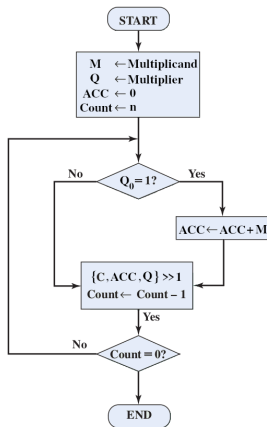
# Sequential Multiplier (Optional)

- Binary multiplication can be done in a sequential manner
- Sequential multiplication is based on two observations
  - Each partial product is either zero or the multiplicand
  - The partial products can be accumulated incrementally
- The process can be described with the following flowchart


 
# Sequential Multiplier (Optional)

- Hardware Architecture
  - M holds the multiplicand
  - Q holds the multiplier
  - A holds the partial products summation



# SystemVerilog Project: Sequential Multiplier (Optional)

- Design a system verilog module to perform the sequential multiplication
- Your module must have the following interface

```
module seq_multiplier (  input  logic [15:0] M,      // 16-bit multiplicand
                        input  logic [15:0] Q,      // 16-bit multiplier
                        input  logic clk,          // Clock signal
                        input  logic reset,        // Reset signal
                        input  logic enable,       // Activate/Deactivate the module
                        output logic [31:0] acc
);

endmodule
```

- The project is optional and has extra bonus
- The following files must be uploaded
  - The multiplier module: *Seq\_Multiplier.sv*
  - Testbench: *Testbench.sv*
  - Simulated Waveforms: *Waveforms.pdf*
  - Comparing the sequential and array multiplier regarding the delay time and resource requirements

## Division (Optional)



- Binary division is based on two basic operations:
  - Generation of partial remainders
  - Subtraction and shifting
- The quotient in division of two  $N$ -bits number is in general a  $N$ -bits number

$$\begin{array}{r} \phantom{1010} 00001110 \\ 1010 \overline{) 10010011} \\ \underline{- 1010} \phantom{0000} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ 10000 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ \underline{- 1010} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ 0110 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ \underline{- 1010} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ 0011 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \end{array}$$

## Division (Optional)

 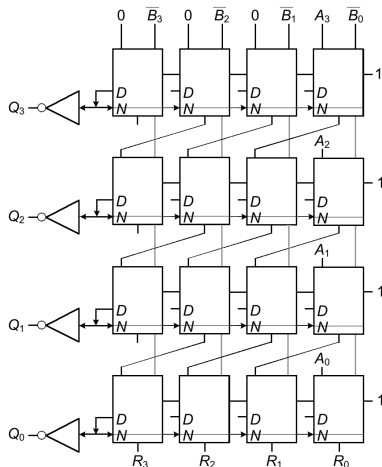
# Array Divider (Optional)

- Hardware implementation of binary division




 
# ALU

- Performs various mathematical and logical operations
- The desired result can be selected by ALUControl


  
# ALU

- Performs various mathematical and logical operations
- The desired result can be selected by `ALUControl`
- An ALU performing `ADD`, `SUB`, `AND` and `OR`





$ALUControl_{2:0}$	Function
000	Add
001	Subtract
010	AND
011	OR


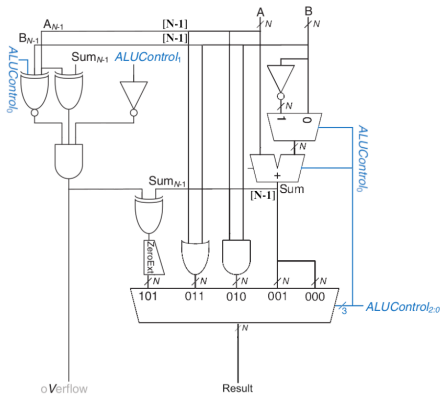 
# ALU



- Performs various mathematical and logical operations
- The desired result can be selected by `ALUControl`
- An ALU performing `ADD`, `SUB`, `AND`, `OR` and `SLT`



$ALUControl_{2,0}$	Function
000	Add
001	Subtract
010	AND
011	OR
101	SLT
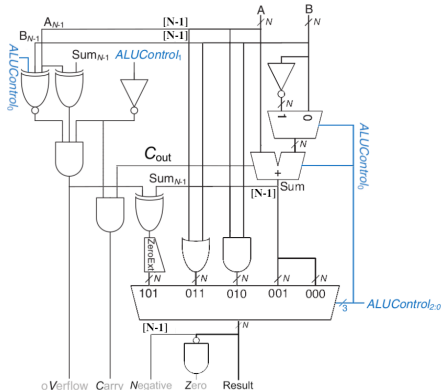 
# ALU

- Performs various mathematical and logical operations
- The desired result can be selected by ALUControl
- An ALU performing ADD, SUB, AND, OR and SLT
- Common flags: Negative, Zero, Carry and oVerflow




ALUControl <sub>2:0</sub>	Function
000	Add
001	Subtract
010	AND
011	OR
101	SLT


# ALU

- Performs mathematical and logical operations
- ALUControl specifies the function
- Common Flags: N, Z, C, V
- Overflow detection
- Comparison depends on signed/unsigned

Comparison	Signed	Unsigned
=	Z	Z
≠	$\bar{Z}$	$\bar{Z}$
<	$N \oplus V$	$\bar{C}$
≤	$Z + (N \oplus V)$	$Z + \bar{C}$
>	$\bar{Z} \bullet (\bar{N} \oplus \bar{V})$	$\bar{Z} \bullet C$
≥	$(\bar{N} \oplus \bar{V})$	C


 


ALUControl <sub>2:0</sub>	Function
000	Add
001	Subtract
010	AND
011	OR
101	SLT

 


# Shifters

- Logical left and right shifts

  
 
# Shifters

- Logical shifter
- Arithmetic shifter
- Arithmetic shift left multiplies by 2
- Arithmetic shift right divides by 2
- Overflow must be taken care of
- N-bit shifter can be built from  $N$ ,  $N : 1$  MUXs



# SystemVerilog (Optional)

- A typical ALU supporting add, sub, and, or, slt, sll, srl
- It has generates Zero and overflow signals

```


module ALU #(parameter N=4, M=3)
    (input logic [N-1:0] a, b,
     input logic [M-1:0] alucontrol,
     output logic [N-1:0] result,
     output logic zero, v;
     logic [N:0] condinvb, sum;
     logic
         isAddSub;

    assign condinvb = alucontrol[0] ? ~b : b;
    assign sum = a + condinvb + alucontrol[0];
    assign isAddSub = ~alucontrol[2] & ~alucontrol[1] |
        ~alucontrol[1] & alucontrol[0];

    always_comb
    case (alucontrol)
        3'b000: result = sum;           // add
        3'b001: result = sum;           // subtract
        3'b010: result = a & b;         // and
        3'b011: result = a | b;         // or
        3'b100: result = a ^ b;         // xor
        3'b101: result = sum[N-1] ^ v; // slt
        3'b110: result = a << b[1:0]; // sll
        3'b111: result = a >> b[1:0]; // srl
        default: result = 4'bx;
    endcase


    assign zero = (result == 32'b0);
    assign v = ~(alucontrol[0] ^ a[31] ^ b[31]) & (a[31] ^ sum[31]) & isAddSub;

endmodule
    
```

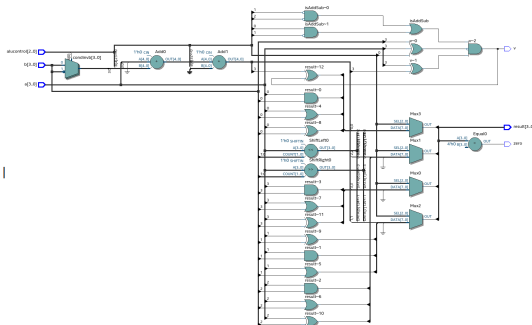

 
# Serial-to-Parallel/Parallel-to-Serial Converters

- Shift registers act as serial-to-parallel converters
- The input is provided serially at  $S_{in}$
- After  $N$  cycles, the last  $N$  inputs appear at  $Q_0 \dots Q_{N-1}$



 
# Serial-to-Parallel/Parallel-to-Serial Converters

- Shift registers act as serial-to-parallel converters
- The input is provided serially at  $S_{in}$
- After  $N$  cycles, the last  $N$  inputs appear at  $Q_0 \dots Q_{N-1}$



 - Shift registers with parallel load can act in reverse
- The input  $D_0 \dots D_{N-1}$  is loaded in parallel
- Takes  $N$  cycles to shift out as parallel-to-serial converter





# Counters

- $N$ -bit counter composed of an adder and a resettable register
- There different approaches for designing various counters
- One easy way is to use an adder
- On each cycle, the counter adds 1 to the value stored in the register
- They are commonly used for dividing the clock frequency

